



FIGURE 3.16 Model of a mixer as an ideal switch. At the top is shown the RF waveform and below that is the state (on or off) of the switch driven at the LO frequency, which is slightly different from that of the RF. The resulting switched output is shown next and is quite messy. However, after the low-pass filter, the difference frequency or beat frequency remains. (Courtesy of Neal Erickson.)